

Peter Wallace
Derek Barbosa
EC413 lab 7

- Task 1: see pre-lab
- Task 2: Implemented a forwarding unit that checks if the Rd in EX/MEM stage is the same as Rs or Rt in ID/EX stage. It then sends out a 2 bit mux signal to the corresponding mux that outputs into the ALU.
- Task 3: Implemented a new part of the forwarding unit that checks if Rd in MEM/WB is the same as Rs or Rt in ID/EX. It also directs the forwarding unit to output a 2 bit mux signal to the corresponding muxA or muxB.
- Task 4: Add a new condition to 2-ahead: as long as Rd in EX/MEM isn't the same as Rd in MEM/WB (and thus requiring a 1 ahead), the 2 ahead mux signals are outputted.
- Task 5: Added logic to the forwarding unit that checks that Rd in EX/MEM isn't equal to 0 for the 1 ahead cases, and MEM/WB for the 2 ahead cases.
- Task 6: Added RegWrite as an input to our forwarding unit. Added conditions in the if statements that checks if RegWrite is = 0 for corresponding cases (1 ahead A/B, 2 ahead A/B).
- Task 7: added a test case to the testbench that uses BEQ (which is a no-write instruction)

